



INDIAN INSTITUTE OF TECHNOLOGY, BOMBAY

MIXED SIGNAL VLSI DESIGN

EE - 719

9-Bit Hybrid Fully Differential ADC

Name :
Abhijeet
G Kamalesh

Roll Number :
20D070003
20D070029

Professor :

Maryam Shojaei Baghini

Feb. 20, 2023

1 Bootstrap Switch Design

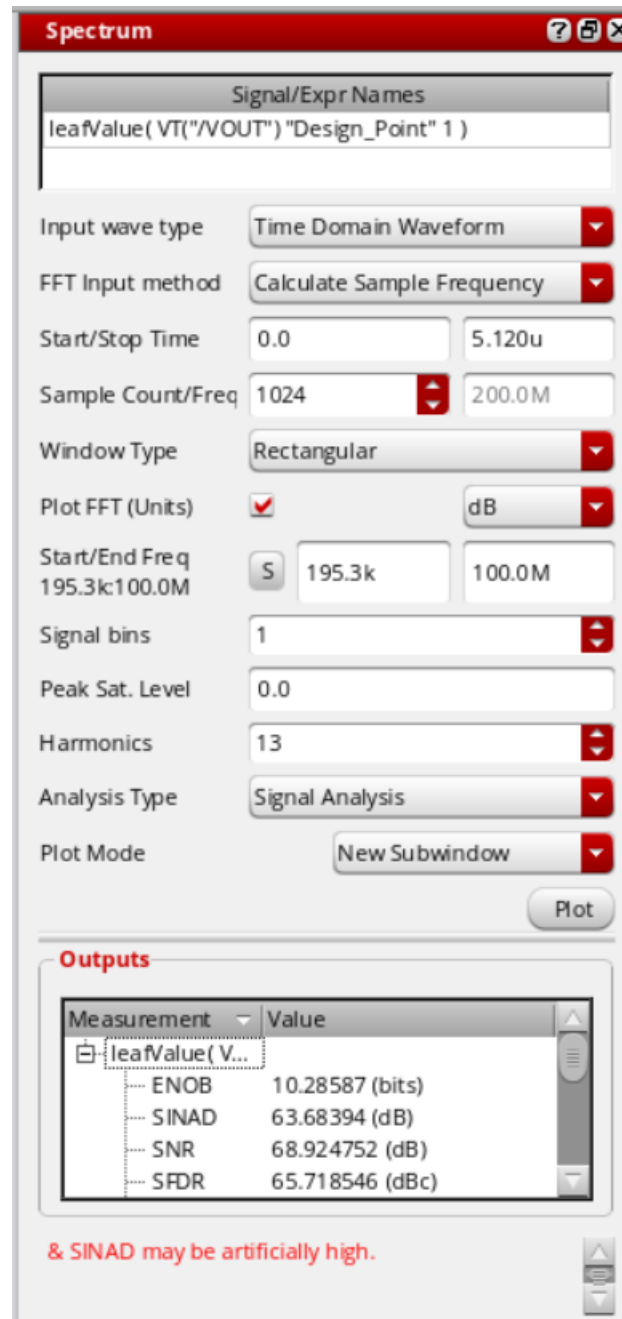


Figure 4: Bootstrap SNR

[1.1] Report the final value of the widths and lengths of all transistors.

Parameter	M_1	M_2	M_3	M_4	M_5	M_6	M_8	M_a	M_b	M_c	C_1	C_B
W(in m)	10μ	500n	500n	320n	1.2μ	750n	320n	675n	375n	600n	90 fF	100 fF
L(in nm)	150	150	150	150	150	150	150	150	150	150	X	X

Table 1: Final Parameter Summary of Bootstrap Switch

2 3-bit differential Flash ADC Design

2.1 Preamplifier design

The preamplifier is a fully differential amplifier designed to produce a gain of 2 before the comparator

 


Figure 5: FFT of Bootstrap output waveform

- As a starting point we assumed to flow a 25 uA current in the tail part of the pre-amplifier.
- For that value of current we tried to find the initial value of the biased transistor such that it will come the saturation region.
- At the Width of 1um and bias voltage of 0.6V. the bottommost transistor is in saturation mode.
- Now we increased the current by increasing widths and of the differential pair and the biased transistors. So that differential paired transistors will be in saturation mode.
- Now our final task is to increase the gain for the worst case more than 2.
- That we achieved by increasing the bias voltage from 0.6V to 0.8 V and slight increments in the widths of the transistor.

Initial parameters

Design Variable	M_1	M_2	M_3	M_4	M_5	M_6	M_7	M_8	R_1	R_2
Width	5um	5um	5um	5um	1um	1m	1um	1um	1K Ω	1K Ω
Length (nm)	150	150	150	150	150	150	150	150		

Table 2: Initial parameters for Preamplifier

Final parameters

Design Variable	M_1	M_2	M_3	M_4	M_5	M_6	M_7	M_8	R_1	R_2
Width	40u	40u	20u	20u	10u	10u	10u	10u	-	-
Length	150n	150n	150n	150n	150n	150n	150n	150n	1k	1k

Table 3: Final parameters for Preamplifier

Please note that the transistor numberings are reversed in the table and the schematic

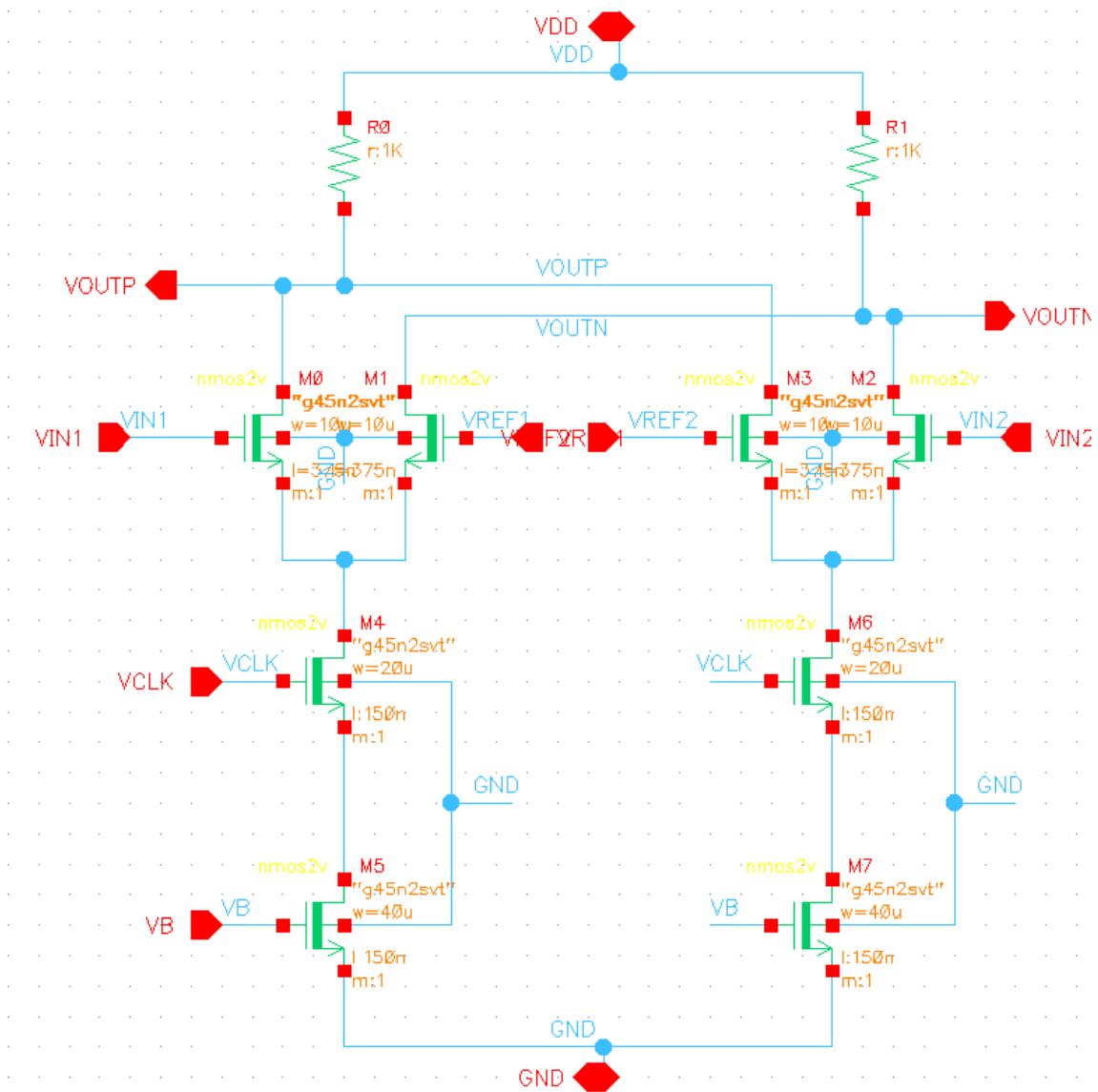


Figure 6: Preamplifier schematic

2.2 Testing of Preamplifier

1. Take $V_{ref1} = 0.9375$ V and $V_{ref2} = 0.5625$ V (worst case reference inputs in the flash ADC) and $V_{inc1} = V_{cm} + 0.25 \sin(2f_{int})$ and $V_{inc2} = V_{cm} - 0.25 \sin(2f_{int})$ and plot the transient output for $f_{in} = 50$ MHz.

 


Figure 7: Preamplifier output waveform

2. Take $V_{ref1} = 0.75$ V and $V_{ref2} = 0.75$ V and $V_{inc1} = V_{cm} + 0.25 \sin(2\pi f_{int})$ and $V_{inc2} = V_{cm} - 0.25 \sin(2\pi f_{int})$ and plot the transient output for $f_{in} = 50$ MHz.

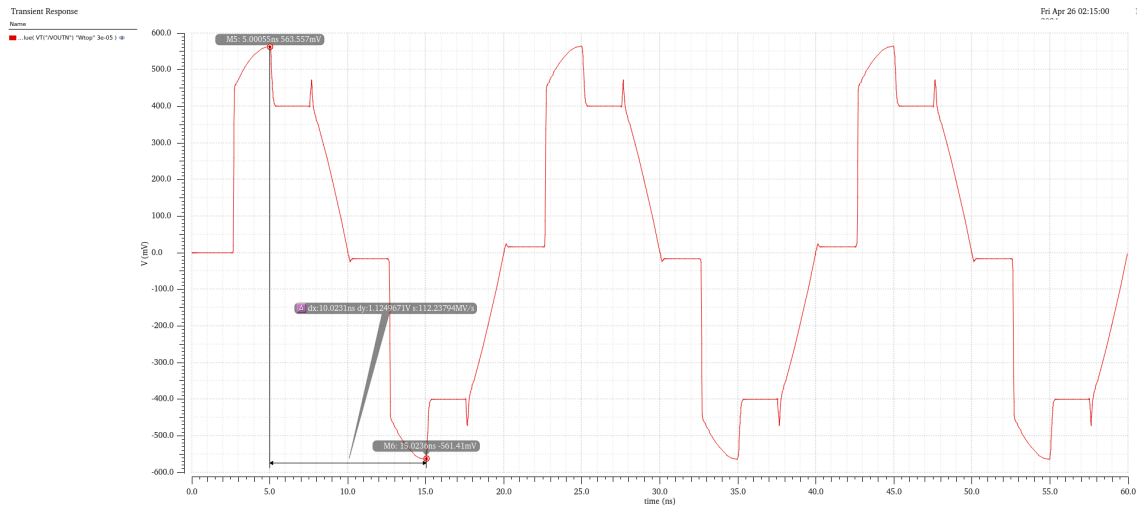


Figure 8: Preamplifier output waveform

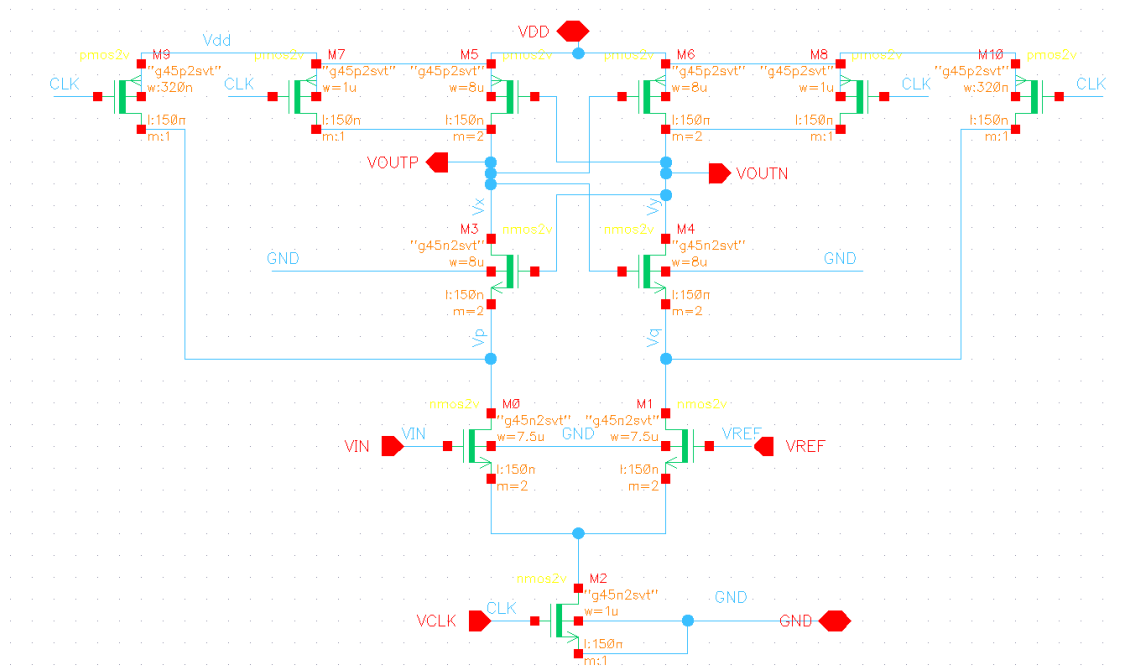


Figure 9: Strong arm Latch Comparator schematic

 


Figure 10: Strong arm Latch Comparator schematic

[illegible]

Table 4: Initial parameters for Preamplifier

[illegible]

Table 5: Final parameters for Preamplifier

 


Figure 11: RS Latch schematic

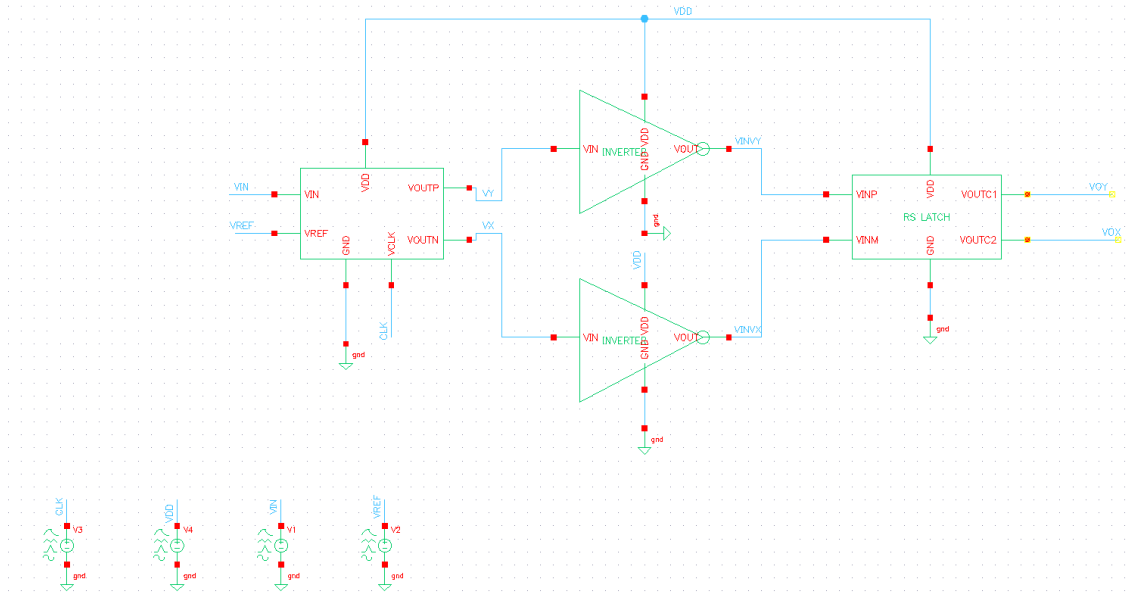


Figure 12: Strong arm Latch Comparator followed by RS Latch Testbench

 


Figure 13: Strong arm Latch followed by RS Latch output waveform

2.4 Differential Flash ADC

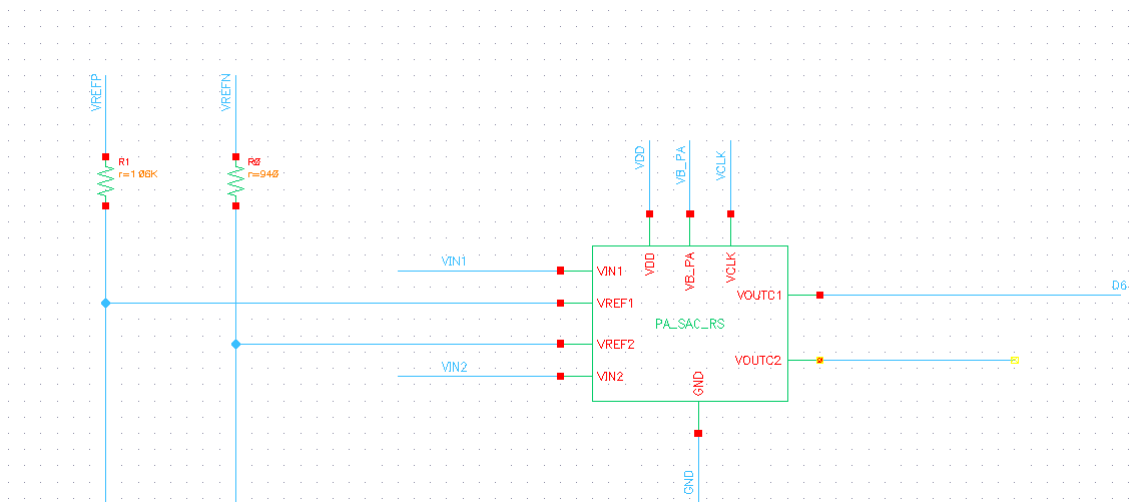


Figure 14: Temperature code generator

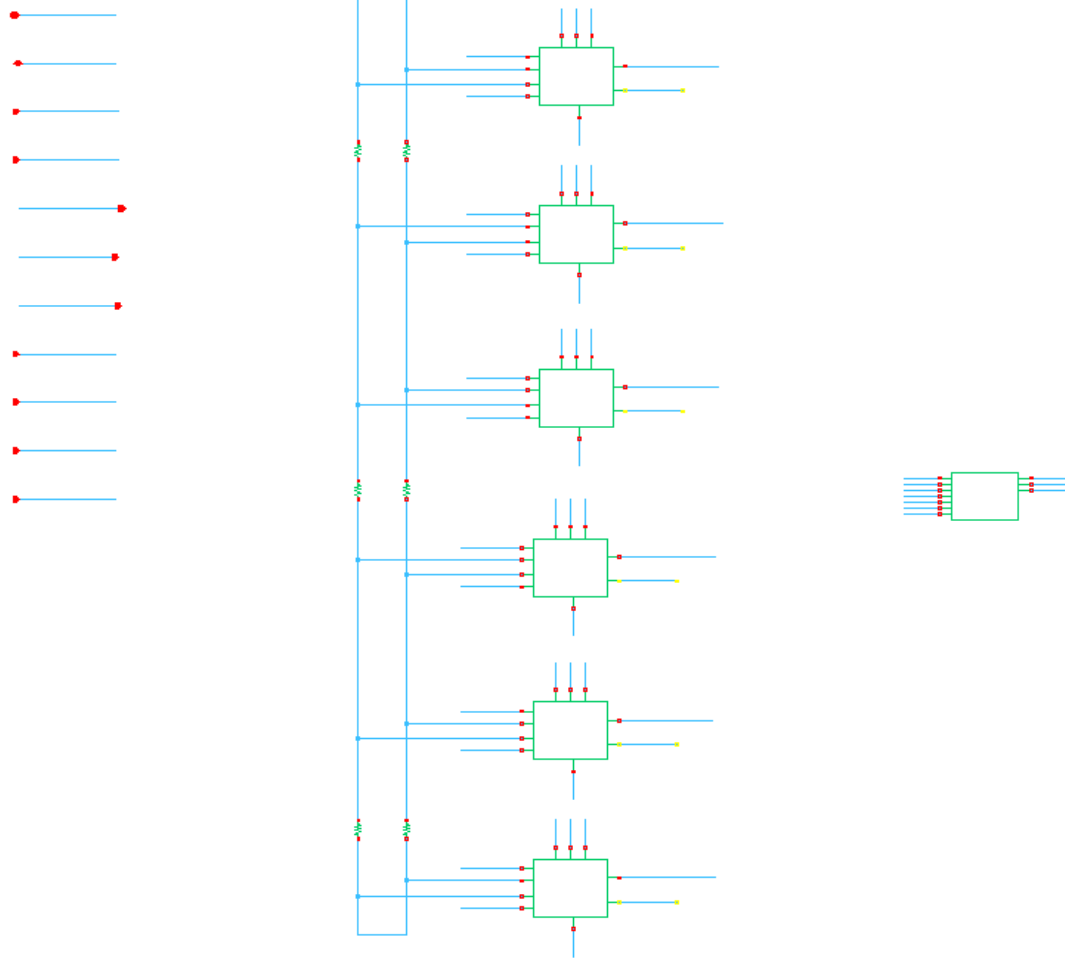


Figure 15: 3 Bit Fully differential Flash ADC

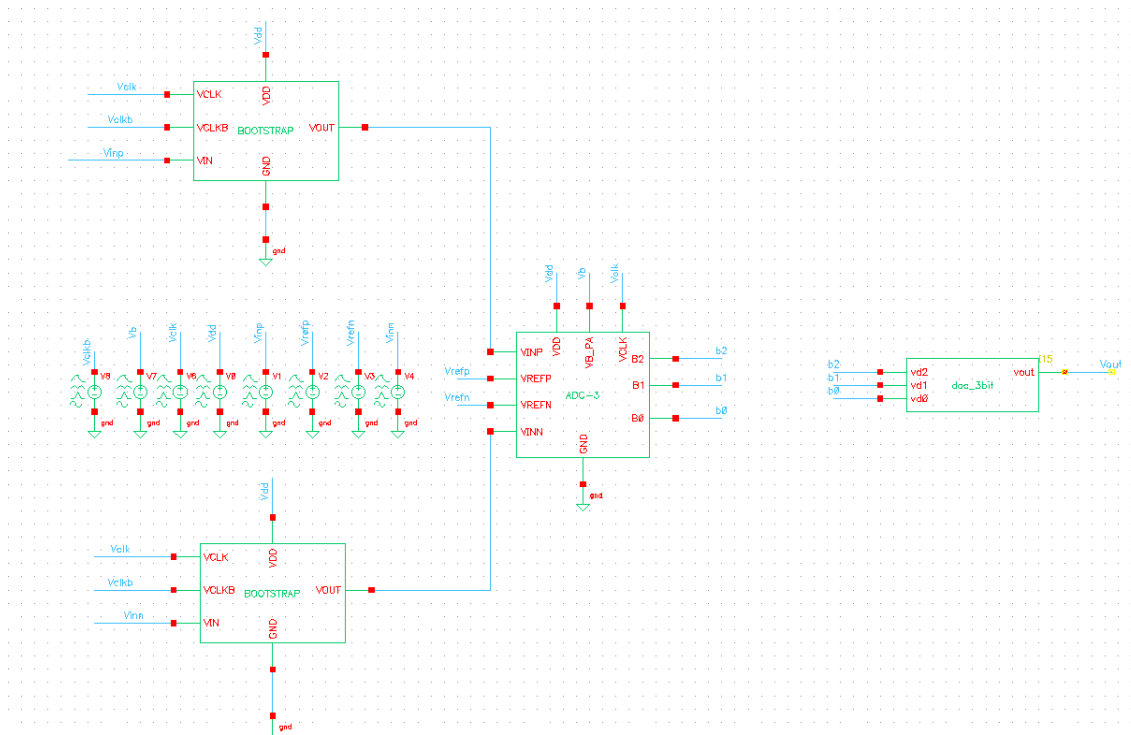


Figure 16: Flash ADC Testbench

2.5 FFT with ADC + ideal DAC topology

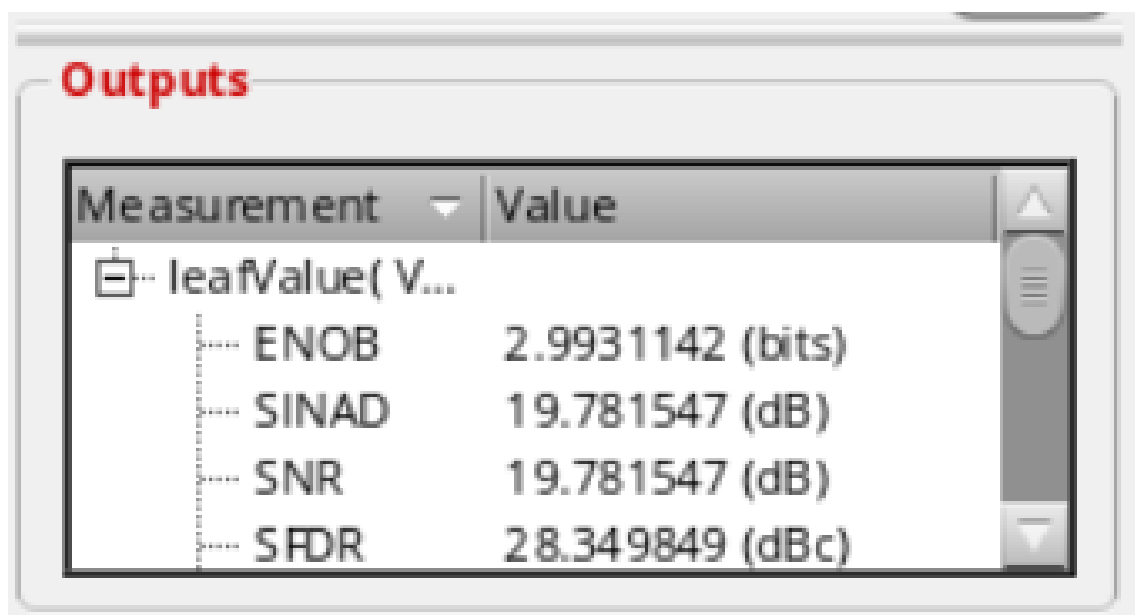


Figure 17: SNR of Flash ADC

 


Figure 18: THD of Flash ADC

2.6 INL DNL - non-linearities in the resistor

The value of R is $1k\ \Omega$ and hence, $\Delta R = 20\ \Omega$. The plots obtained by providing a ramp signal at the input are attached below:

 


Figure 19: DAC Output vs Input characteristics

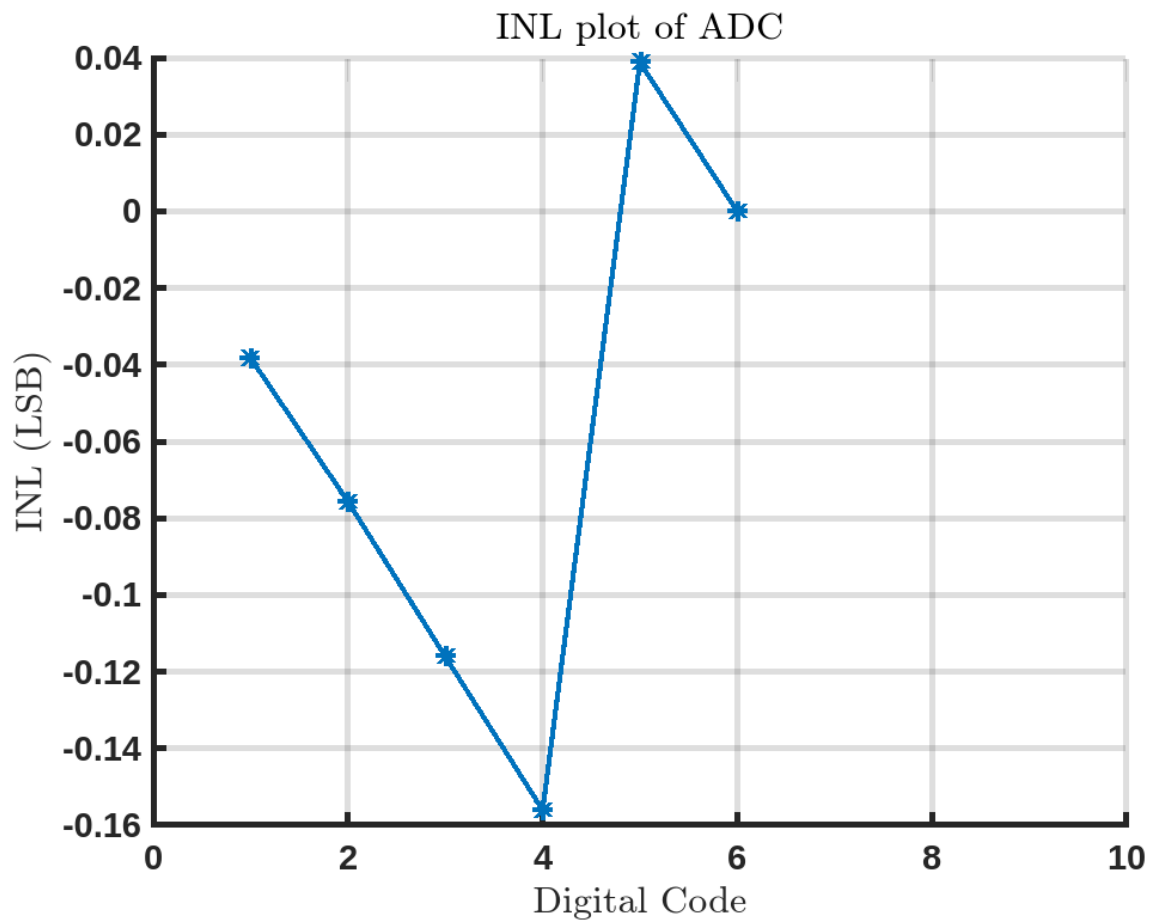


Figure 20: INL

 


Figure 21: DNL

Parameters	Values
Supply Voltage (V_{DD})	1.5 V
Input Voltage Swing (V_{FS})	0.5 – 1.0 V
Number of Bits (N)	3
Sampling Frequency	200 MHz
Temperature	27°C
Clock rise, fall time	20 ps

Figure 22: Specifications of SAR ADC

3 Design of 6-bit Differential SAR ADC

3.1 Comparator + RS Latch

In this section, you need to design a latched comparator for the fine ADC. The Report the design procedure followed and tabulates the initial and final dimensions of all the transistors. Ensure that the comparator's outputs are settling within a half-clock cycle.

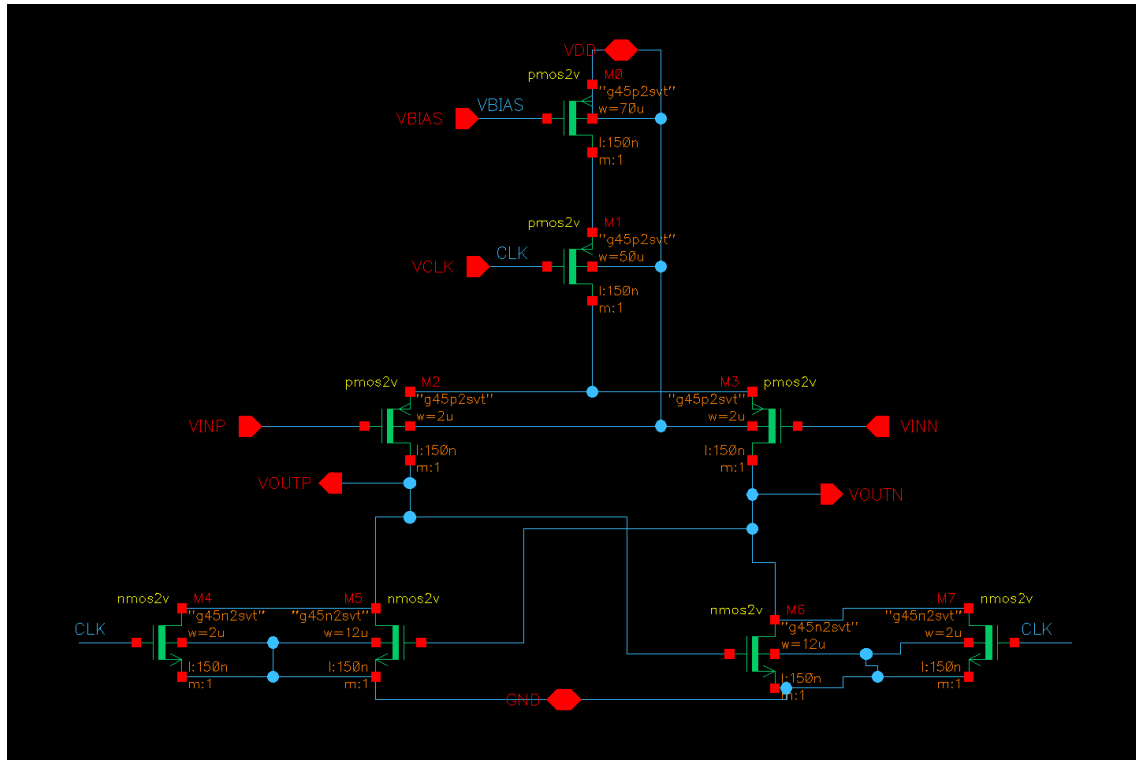


Figure 23: PMOS Strong Arm Latch Comparator Schematic

Design Variable	M_1	M_2	M_3	M_4	M_5	M_6	M_7	M_8
Width	70u	50u	2u	2u	2u	12u	12u	2u
Length	150n	150n	150n	150n	150n	150n	150n	150n

Table 6: Final parameter summary of PMOS Strong ARM latch comparator

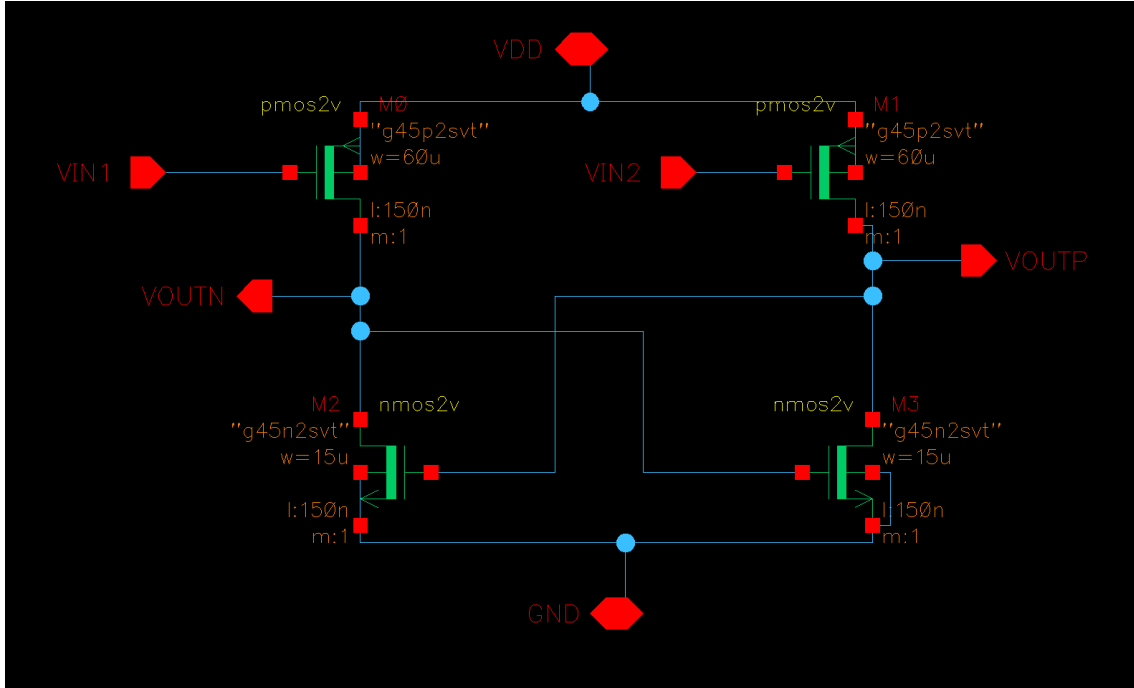


Figure 24: RS Latch Schematic

 


Figure 25: RS Latch output waveform

Design Variable	M_{P1}	M_{N1}	M_{P2}
M_{N2}			
Width 15u	60u	15u	60u
Length 150n	150n	150n	150n

Table 7: Final parameters for Preamplifier

3.2 Binary weighted charge redistribution capacitive DAC

1. Choose an appropriate unit capacitance value for the C-DAC considering the SNR requirements. Justify the capacitance value chosen in the report. SNR of the Sampler-ADC cascade is,

$$SNR = \frac{\frac{A^2}{2}}{\frac{\Delta^2}{2} + \frac{KT}{C_1}} \quad (1)$$

$$\text{Ideal SNR} = 56 \text{ dB} = 10 \log\left(\frac{\frac{A^2}{2}}{\frac{\Delta^2}{2}}\right) \Rightarrow \frac{\Delta^2}{A^2} = 10^{-6.2}$$

$$\text{Degraded SNR} = 56 - 2 = 54 \text{ dB.}$$

$$SNR = 54 \text{ dB} = 10 \times \log\left(\frac{\frac{A^2}{2}}{\frac{\Delta^2}{2} + \frac{KT}{C_1}}\right) \quad (2)$$

$$C_1 = 90 \times 10^{-15} \quad (3)$$

Since the SAR ADC is fully differential, the capacitance C1 would be twice C1. Therefore, C1 = 180 fF. We took $C_1 = \mathbf{217 \text{ fF}}$.

2. To introduce nonideality in the capacitor values, use the MATLAB script provided to generate the values of the 5 capacitances to be used. You need to input your group number and the chosen value of the unit capacitance. Use the same capacitances for C-DACs on both sides of SAR ADC (e.g. C1p = C1n).

We had assumed the mean value of unit capacitance to be 7 fF and our group number is 5. The corresponding capacitance values(in fF) are 6.9760, 14.2333, 27.7853, 57.4759, and 111.9812.

3.3 SAR Logic

 


Figure 26: SAR Logic Schematic

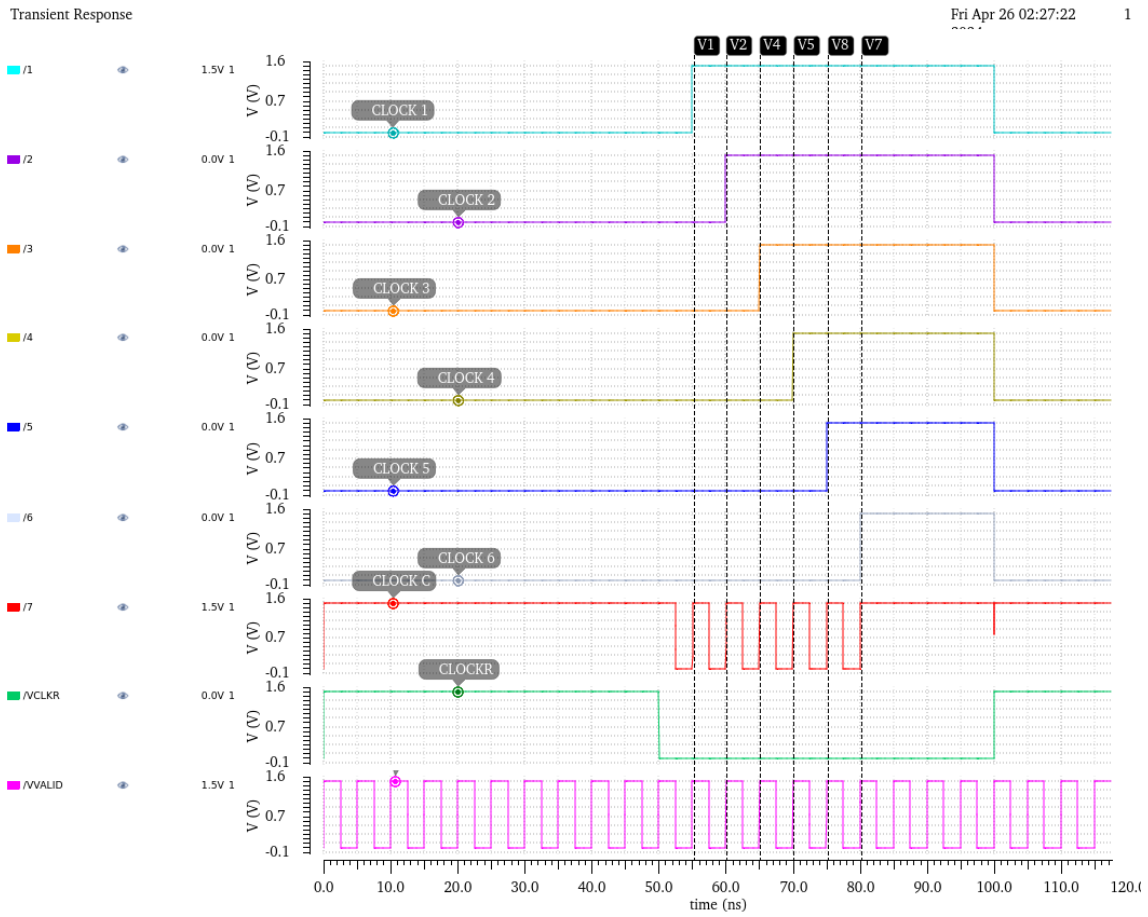


Figure 27: SAR Logic

 


Figure 28: SAR Logic

 


Figure 29: SAR Logic

(a) **Monotonic Switching:**

Plot the waveforms of V_{inp} and V_{inn} (inputs to the comparator of SAR ADC), showing the reduction in range due to the monotonic switching scheme for the complete SAR conversion cycle (6 clock cycles), for inputs - 0.64V (V_{inp}) and 0.72V (V_{inn}).

 


Figure 30: Input waveform monotonic switching

 


Figure 31: Output waveform monotonic switching

(b) **Output waveform:**

Use the provided ideal 6-bit DAC at the outputs of the SAR ADC. Apply a differential input ramp as shown in Fig. 6 (b) for 800 clock cycles. Plot Output (after DAC) versus Input (differential ramp) characteristics of the ADC.

 


Figure 32: DAC output waveform characteristics of SAR ADC

- (c) **INL DNL** Using the same applied inputs in part (b), for the obtained output characteristics, plot the INL and DNL of the ADC versus code using the MATLAB code provided.

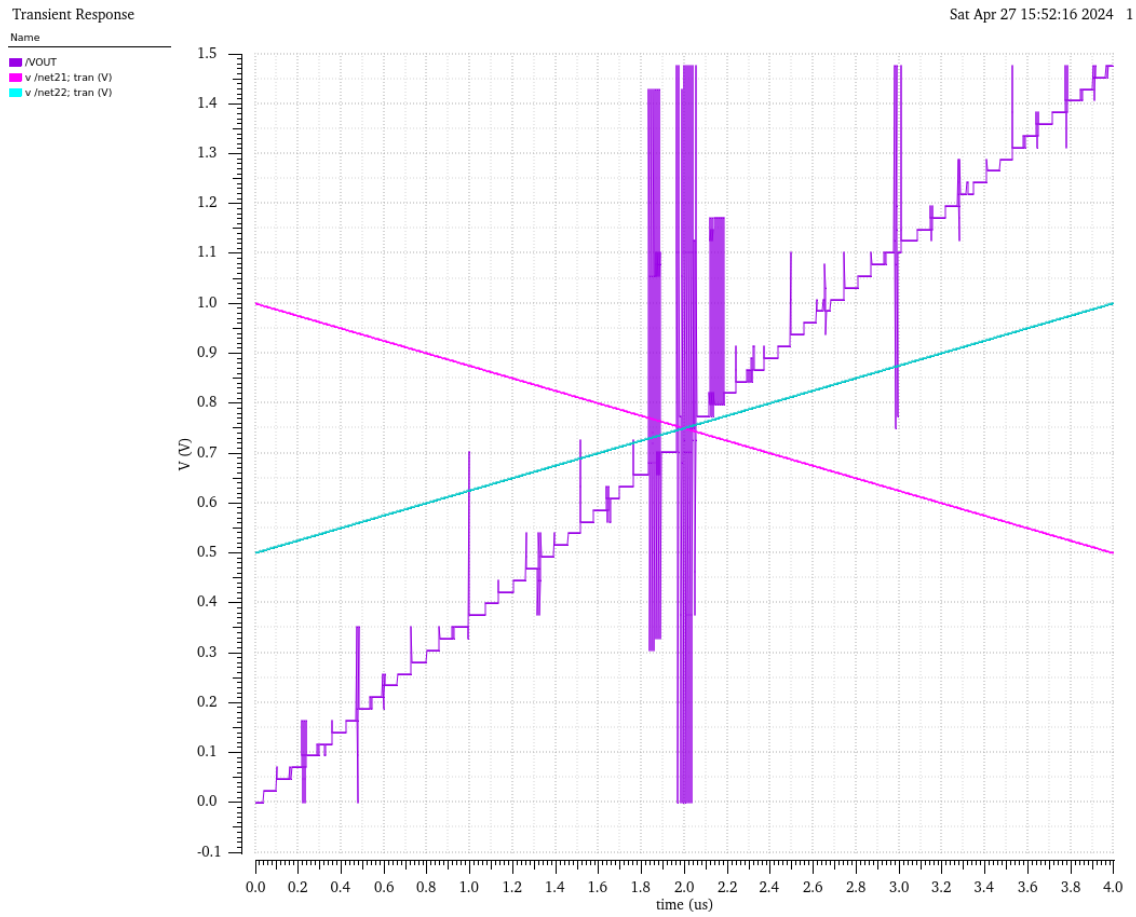


Figure 33: Output characteristics of Ramp input

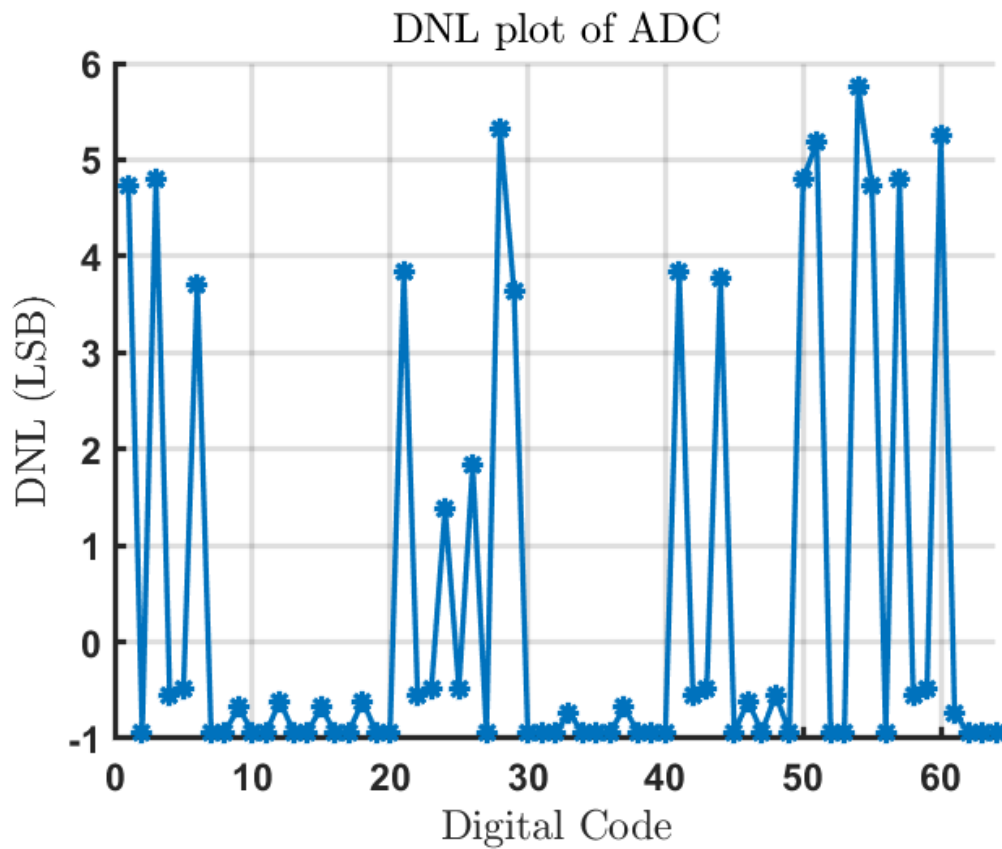


Figure 34: DNL plot of SAR ADC

 


Figure 35: INL plot of SAR ADC

- (d) **FFT, SNR ENOB:** To the circuit shown in Fig. 11, apply $V_{in1} = 0.75 + 0.25 \sin(2\pi f_{int})$ and $V_{in2} = 0.75 + 0.25 \sin(2\pi f_{int})$ with $f_{in} = m \cdot f_s / N$, $m = 511$, $N = 1024$ and plot FFT of the V_{out} . Annotate the fundamental, 2nd and 3rd harmonic components and calculate ENOB, SNR.

db20(dft(leafValue(VT("/VOUT") "delay" 4e-11) 0.01u 5.13u 1024 "Rectangular" 0 0 1))

4

 


Figure 36: FFT of output waveform for SAR ADC

 


Figure 37: FFT of output waveform for SAR ADC

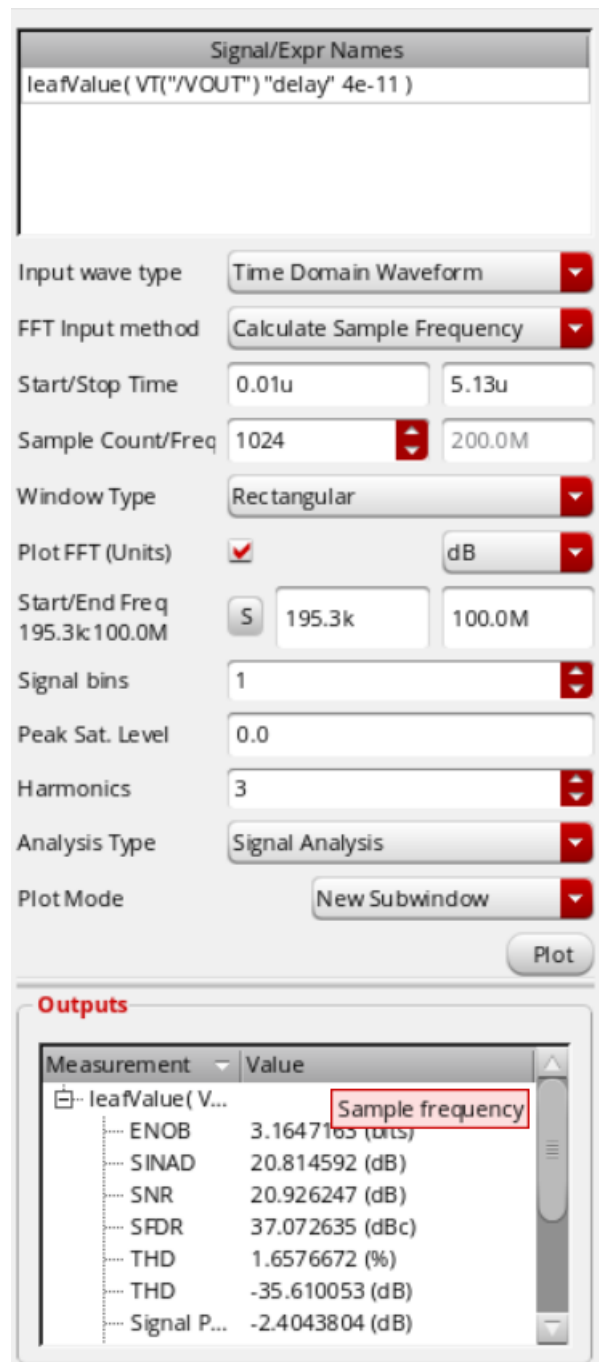


Figure 38: FFT of output waveform for SAR ADC

4 Hybrid 9-bit ADC

4.1 Thermometer-coded Charge distribution capacitive DAC for flash-ADC

The thermometer-coded output of the Flash ADC will be used to drive capacitive DAC. As the unit capacitance of the SAR ADC is $C = 7 \text{ fF}$. the flash ADC, since it's a 3-bit ADC, it provides 8 possible voltage levels. We allocate 3 capacitors to represent the voltage differences between these levels. Each capacitor should cover a unique voltage range. These capacitors each represent 1 bit of resolution, they can be considered equivalent in value. Therefore, each can have the same capacitance value, which we'll designate as "C".

$$C_{1n,p-7n,p} = C = 7fF \quad (4)$$

Values Calculate using the MATLAB Code:

- 1) 6.9760
- 2) 7.1166
- 3) 6.9463
- 4) 7.1845
- 5) 6.9988
- 6) 7.0213
- 7) 7.0479

4.2 FFT, SNR and ENOB

To the circuit shown in figure 12, apply $V_{in1} = 0.75 + 0.25 \sin(2f_{in}t)$ and $V_{in2} = 0.75 \sin(2f_{in}t)$ with $f_{in} = m \cdot \text{fs}/N$, $m = 511$, $N = 1024$ and plot FFT of the V_{out} . Annotate the fundamental, 2^{nd} and 3^{rd} harmonic components and report ENOB, SNR

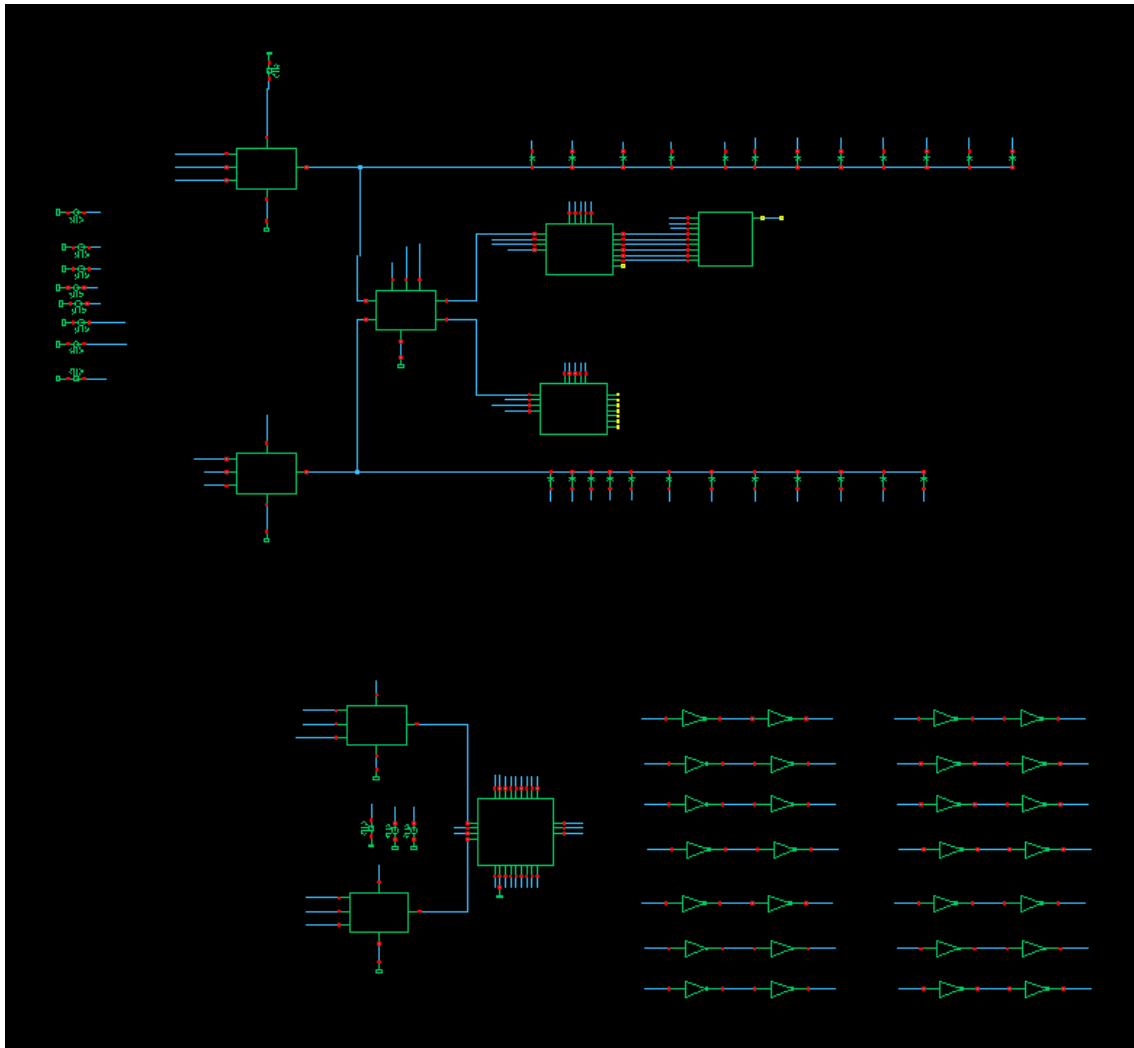


Figure 39: Schematic Diagram

 


Figure 40: Output waveform

 


Figure 41: FFT

Signal/Expr Names
leafValue(VT("/VOUT") "delay" 4e-11)

Input wave type: Time Domain Waveform

FFT Input method: Calculate Sample Frequency

Start/Stop Time: 0.04u 5.16uu

Sample Count/Freq: 1024 200.0M

Window Type: Rectangular

Plot FFT (Units): ☒ dB

Start/End Freq: 5 195.3k 100.0M

Signal bins: 1

Peak Sat. Level: 0.0

Harmonics: 3

Analysis Type: Signal Analysis

Plot Mode: Replace

Plot

Outputs

Measurement	Value
leafValue(V...	
..... ENOB	3.3602369 (bits)
..... SINAD	21.991626 (dB)
..... SNR	22.172356 (dB)
..... SFDR	35.090823 (dBc)
..... THD	2.7972368 (%)
..... THD	-31.065415 (dB)
..... Signal P...	-2.1526839 (dB)

Figure 42: SNR and ENOB

5 Work Contribution

Question Number	Abhijeet	G Kamalesh
1		✓
2-1	✓	
2-2	✓	
2-3	✓	
2-4		✓
2-5		✓
2-6		✓
3-1	✓	
3-2		✓
3-3	✓	
3-4	✓	✓
4-1	✓	✓
4-4	✓	✓

Table 8: Work Distribution